

pgs. 1-2:

- Voltage
- Direct current (DC)
- Alternating Current (AC)
- Amperes (amps), A
- $\Omega$ , Resistance
- Increases, Decreases

- Current
- Ohm's Law
- Parallel
- Current
- Parallel
- Parallel

- Series
- Ammeter, Voltmeter
- Conductor, Insulator
- Potentiometer
- Short Circuit
- Power
- Kilowatt-hours

Current	I	Amperes	A
Voltage	V	Volts	V
Resistance	R	Ohms	$\Omega$
Power	P	Watts	W
Electrical Energy	E	Joules	J


pgs. 3-4:

$R_{TOT} = 4\Omega$ $I_A = 5A$ $I_B = 5A$ $V_{R1} = 10V$ $V_{R2} = 10V$	$R_{TOT} = 3\Omega$ $I_A = 4A$ $I_B = 4A$ $V_{R1} = 4V$ $V_{R2} = 8V$	$V_{R1} = 12V$ $V_{R2} = 12V$ $R_{TOT} = 3\Omega$ $I_A = 4A$ $I_B = 2A$ $I_C = 2A$	$V_{R1} = 30V$ $V_{R2} = 30V$ $R_{TOT} = 6\Omega$ $I_A = 3A$ $I_B = 2A$ $I_C = 5A$
---	---	---	---

↔ Series      ↔ Parallel

pgs. 5-6:

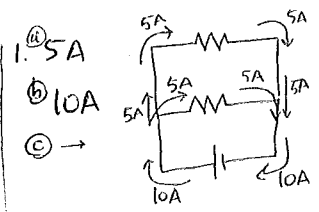- $I = 3A$
- $6\Omega, 1A$
- $12\Omega$
- @ Circuit B
  - @ Circuit A
  - @  $4 \neq 6 =$  brightest
  - @  $1, 2, 3 =$  dimmest ( $5 =$  off)
  - @  $4 \neq 6$
  - @ Circuit B has more current, (both have the same voltage), so B has more power.
  - @ Circuit B! (More Watts).



- 10A
  - 10A
  -
- D is not equivalent
- @ 20V
  - i. 4A
  - ii. 4A
  - iii. 2A
- @ 10A
- @  $\frac{1}{R_{TOT}} = \frac{1}{5} + \frac{1}{5} + \frac{1}{10} = \frac{5}{10}$
- @  $R_{TOT} = \frac{10}{5} = 2\Omega$


pgs. 7-8:

- $R_{TOT} = 4.4\Omega$
  - $I = 1.36A$
  - $6V$
  - $I_{R1} = I_{R2} = 0.6A$   
 $I_{R3} = 0.75A$
  - $P_{R1} = P_{R2} = 3.6W$   
 $P_{R3} = 4.5W$
- $R_{1,2} = 4\Omega$
  - $R_{TOT} = 7.5\Omega$
  - $R_x = 3.5\Omega$
  - $V_{R_x} = 1.4V$   
 $V_{R1} = V_{R2} = 1.6V$
  - If  $R_x \uparrow$ , the total resistance of the circuit increases, so the current decreases.

- $R_{TOT} = 5.7\Omega$
  - $I_B = 1.58A$  ←  $c. I_{R1} = 1.58A$
  - $V_{R1} = 7.11V$   
 $V_{R2} = V_{R3} = 1.89V$
  - $I_{R2} = 0.63A$   
 $I_{R3} = 0.95A$
- $R_{3,4} = 2\Omega$     $R_{2,3,4} = 5\Omega$  }  $R_{2,3,4} = 2.5\Omega$   
 $R_{5,6} = 3\Omega$     $R_{5,6,7} = 5\Omega$  }  
 $R_{TOT} = 12.5\Omega$
  - $I_B = 2A$
  - $I_{R7} = 1A$
  - $V_{R7} = 2V$
  - If  $R_1$  gets  $V_{R1} = I_B \cdot R_{R1} = (10)(2) = 20V$  then branch  $5,6,7$  gets  $5V$ . And if  $R7$  uses  $2V$ , then both  $R_5 \neq R_6$  get  $3V$ .
  - $I_{R6} = \frac{3V}{12\Omega} = 0.25A$

pgs. 9-10:

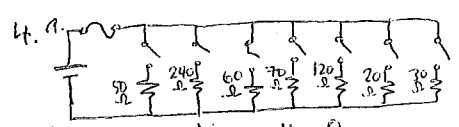- $24W$
- $960W$
- $0.625A$
- $R = 24\Omega$
  - $P = 600W$
  - $P = 0.6W$
- $5kW$
  - $10kWh$
  - $\$1.50$
- $300min$
  - $5hrs$
  - $1.2kW$
  - $6kWh$
  - $\$0.90$
- $20.45A$
  - $10.76\Omega$
  - $4.5kW$   
 $10kWh$
  - $\$140.40$




- The fuse blows the fuse
- The heater trips the circuit breaker

pgs. 11-12:

1. A fuse is a wire that breaks when too much current flows. This protects your wires because it will blow before the wiring lights on fire!

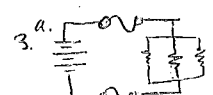2. In a series circuit, more resistors decreases the current flow. (no fuse needed!)



- Just under  $600W$
- Just under  $225W$